



Electrical Circuits


Section 7.3



Components of a circuit


- Source of voltage difference (provided by a battery or an outlet)
- At least one device that uses electrical energy (radio, microwave, clock, fan, etc)
- Conductor (like wire) that connects the device to the source of voltage difference

Simple Series Circuit

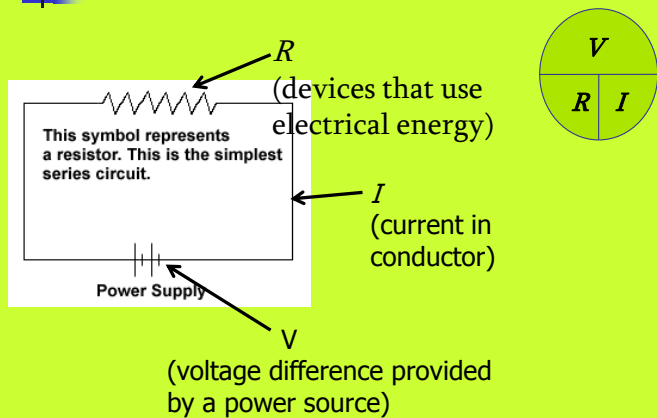


Open Series Circuit

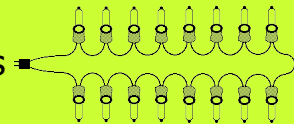- Parts are wired one after another with the same current running through every part
- If one part of a series circuit is disconnected, then no current will flow through the circuit
- String of Christmas lights




Simple Series Circuit

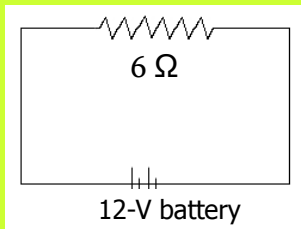Calculate the flow of current through the following circuit.



$$I = \frac{12 \text{ Volts}}{6 \text{ ohms}}$$

$$I = 2 \text{ amps}$$

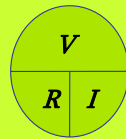

Simple Series Circuit

Calculate the total resistance of the circuit.

$$R_{\text{total}} = R_1 + R_2 + R_3 + R_4$$

$$R_{\text{total}} = 2 \Omega + 2 \Omega + 2 \Omega + 3 \Omega \quad R_{\text{total}} = 9 \Omega$$


Calculate the current leaving the battery.

$$I = \frac{12 \text{ Volts}}{9 \text{ ohms}} \quad I = 1.33 \text{ amps}$$



Calculate the current through each resistor.

$$I = 1.33 \text{ amps}$$

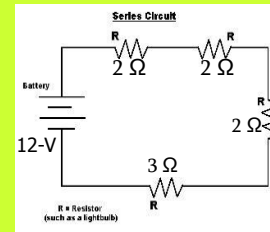"same current running through every part"



Simple Series Circuit

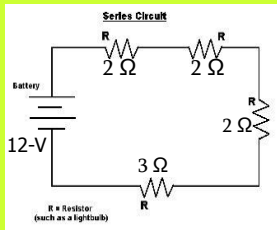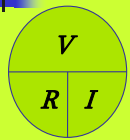

Calculate the voltage drop through each resistor.

For R_1, R_2, R_3

$$V = (2\Omega)(1.33 \text{ amps})$$

$$V = \mathbf{2.67 \text{ volts}}$$

For R_4

$$V = (3\Omega)(1.33 \text{ amps})$$

$$V = \mathbf{3.99 \text{ volts}}$$


Check:

The sum of the voltage drops equals the voltage total supplied by the power source.

$$V_{\text{total}} = 2.67 \text{ V} + 2.67 \text{ V} + 2.67 \text{ V} + 3.99 \text{ V}$$

$$V_{\text{total}} = \mathbf{12 \text{ volts}}$$

Practice

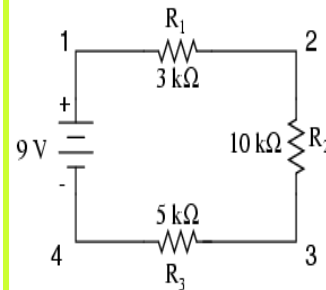


Calculate the total resistance of the circuit.

Calculate the current leaving the battery.

Calculate the current through each resistor.

Practice

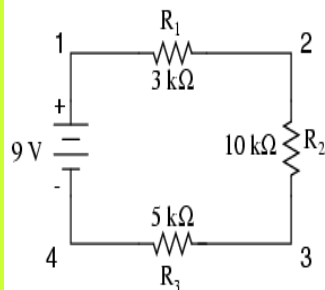

Calculate the voltage drop through each resistor.

Check:
The sum of the voltage drops equals the voltage total supplied by the power source.


Parallel Circuits

- A type of circuit that has more than one path for current is called a parallel circuit.
- Contains two or more branches for the current to move through



Parallel Circuit Advantages

- If one part of the path is removed, the current continues to flow through the other paths of the circuit.
- If you turn off the light the current continues to flow through the other branches.
- If you add resistance it doesn't affect the flow of current to the other branches

Parallel Circuit

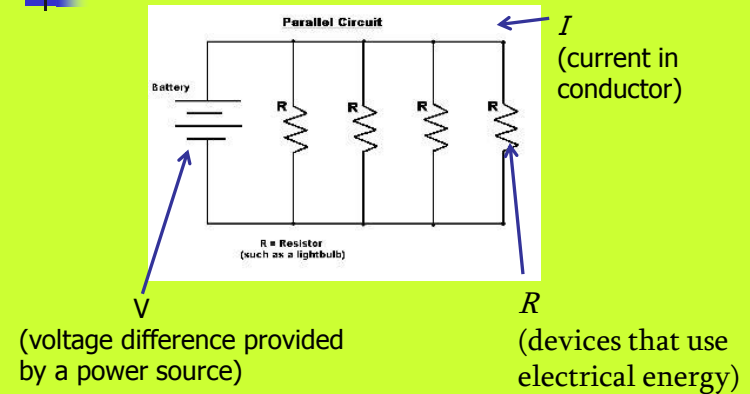

Parallel Circuit

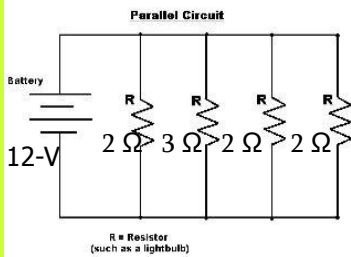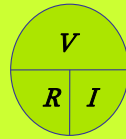

Calculate the current through each resistor.

For R_1, R_3, R_4

$$I = \frac{12 \text{ Volts}}{2 \text{ ohms}}$$

$$I = 6 \text{ amps}$$

For R_2

$$I = \frac{12 \text{ Volts}}{3 \text{ ohms}}$$

$$I = 4 \text{ amps}$$

Calculate the total current of the circuit.


$$I_{\text{total}} = I_1 + I_2 + I_3 + I_4$$

$$I_{\text{total}} = 6 \text{ amps} + 4 \text{ amps} + 6 \text{ amps} + 6 \text{ amps}$$

$$I_{\text{total}} = 22 \text{ amps}$$



Practice

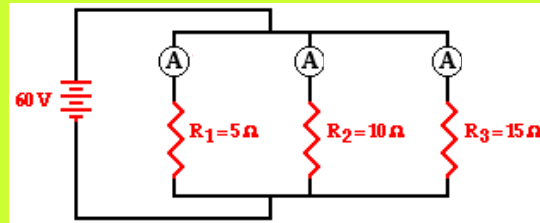Calculate the current for each of the different resistors.



You should notice that the current is greatest where the resistance is least and the current is least where the resistance is greatest.



Parallel Circuit

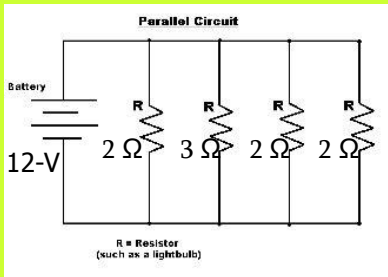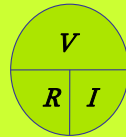

Calculate the voltage drop through each resistor.

There is no voltage drop, each branch is the same (equal to the total voltage difference of 12 volts).

Parallel Circuit

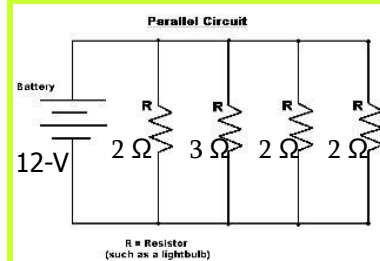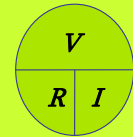

Calculate the Equivalent Resistance

Since the circuit offers four pathways for charge flow, only a portion of the charge will *pass* through a given branch.


$$R_{\text{eq}} = \frac{V}{I_{\text{total}}}$$

$$R = \frac{12\ \text{volts}}{22\ \text{amps}}$$


$$R_{\text{eq}} = 0.55\ \text{ohms}$$

Practice

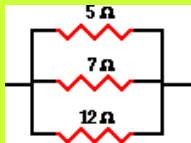A $5.0\ \Omega$, $7.0\ \Omega$ and $12\ \Omega$ resistor are placed in parallel, calculate the equivalent resistance.



Practice

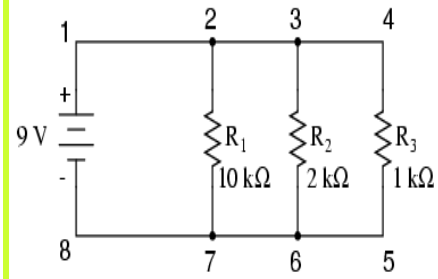


Calculate the current through each resistor.

Calculate the total current of the circuit.



Practice

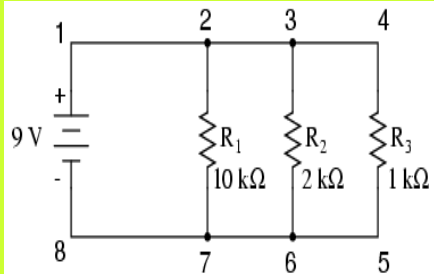

Calculate the Equivalent Resistance