

Warm Up

A toy car has a maximum power of 23.0 W when it is hooked up to a 9.0 V battery.

1) How much current is the car drawing?

2) What is the resistance of the car?

