

Warm UP

Refer to the diagram below.

1. What type of battery is shown (*dry-cell* or *wet-cell*)?
2. Identify the resistance, the current and the voltage.
3. What direction does the current flow?

