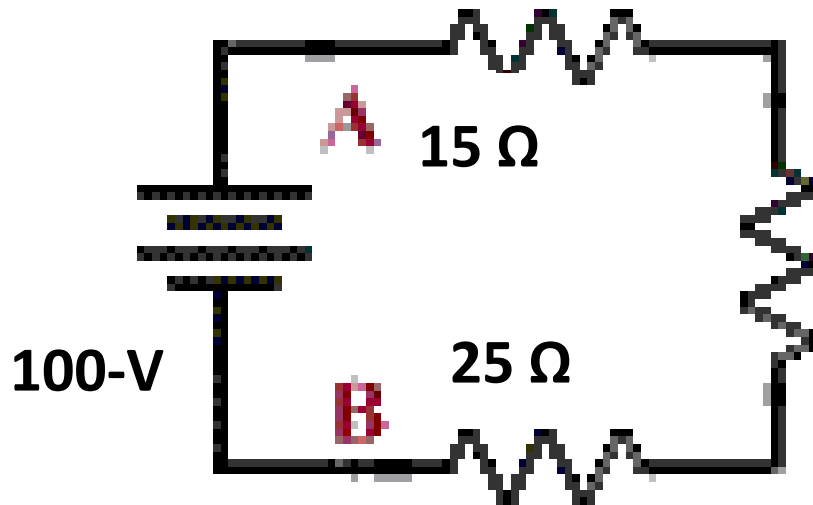



Warm Up



What is the total resistance?

What is the total current?

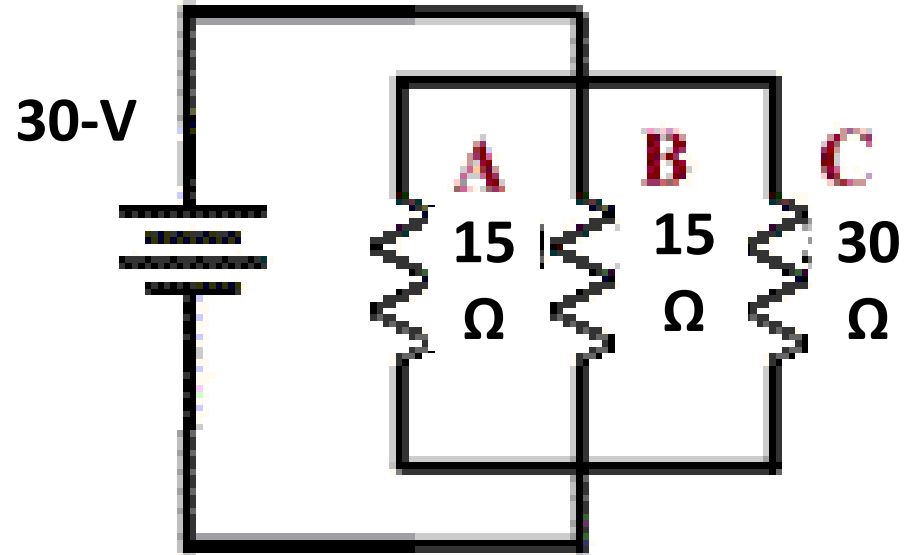What is the voltage drop through each resistor?



What is the current through each resistor?

What is the total current in the circuit?

What is the equivalent resistance of the circuit?