

Warm Up Determine the total current and equivalent resistance for each of the circuits shown below.

