

WARM UP

A nine volt battery supplies power to a cordless curling iron with a resistance of 18 ohms. How much current is flowing through the curling iron?



A 110 volt wall outlet supplies power to a strobe light with a resistance of 2.2 k Ω . How much current is flowing through the strobe light?